

A. 组合逻辑电路

一、 8-3 编码器

1. 代码实现

```
module biancode(x,y);
    input [7:0] x;
    output reg [2:0] y;
    always@(x)
        begin
            case(x)
                8'b00000001: y = 3'b000;
                8'b00000010: y = 3'b001;
                8'b00000100: y = 3'b010;
                8'b00001000: y = 3'b011;
                8'b00010000: y = 3'b100;
                8'b00100000: y = 3'b101;
                8'b01000000: y = 3'b110;
                8'b10000000: y = 3'b111;
            endcase
        end
endmodule
```

2. 仿真程序及结果

不断改变输入，查看输出是否为预期结果


```
module try();
    reg [7:0] in;
    wire [2:0] out;

    biancode one(in,out);


    initial
        begin
            in = 8'b00000001;
            #100;
            in = 8'b00000010;
            #100;
            in = 8'b00000100;
            #100;
            in = 8'b00001000;
            #100;
            in = 8'b00010000;
            #100;
            in = 8'b00100000;
            #100;
            in = 8'b01000000;
            #100;
            in = 8'b10000000;
            #100;

            in = 8'b00010000;
            #100;
            in = 8'b00100000;
            #100;
            in = 8'b01000000;
            #100;
            in = 8'b10000000;
            #100;

             $finish;
            $stop;
        end
endmodule
```



3. 电路分析

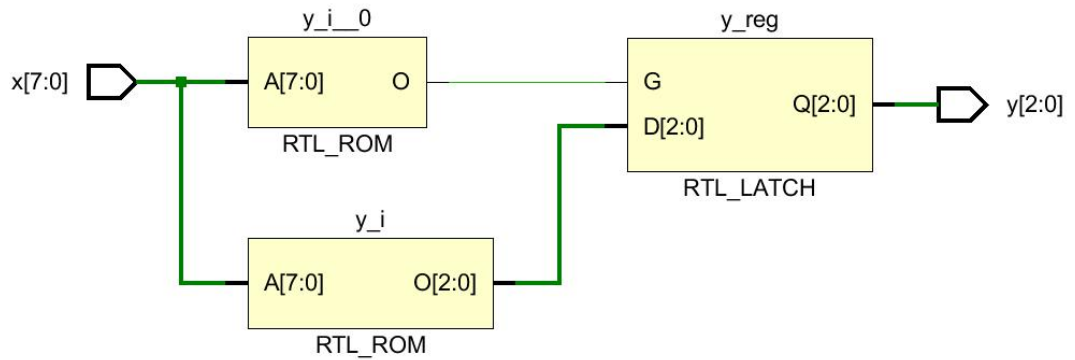

4. 能耗分析

能耗大多消耗在 I/O 上


Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.439 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 27.2°C
 Thermal Margin: 57.8°C (11.5 W)
 Effective θ_{JA} : 5.0°C/W
 Power supplied to off-chip devices: 0 W
 Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 


5. 资源分析

资源利用不多

Summary

Resource	Utilization	Available	Utilization %
LUT	5	20800	0.02
FF	3	41600	0.01
IO	11	106	10.38

 

二、 3-8 译码器


1.代码实现

```
module yicode(in, out);  
    input [2:0] in;  
    output reg[7:0] out;  
    always@(in)  
    begin  
        case(in)  
            3'b000: out = 8'b00000001;  
            3'b001: out = 8'b00000010;  
            3'b010: out = 8'b00000100;  
            3'b011: out = 8'b00001000;  
            3'b100: out = 8'b00010000;  
            3'b101: out = 8'b00100000;  
            3'b110: out = 8'b01000000;  
            3'b111: out = 8'b10000000;  
        endcase  
    end  
endmodule
```

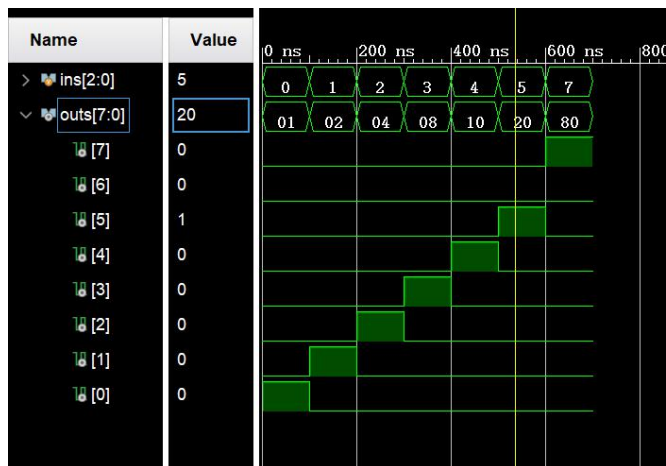
2.仿真代码及结果

不断改变输入，查看输出是否为预期结果


```
module try();  
    reg [2:0] ins;  
    wire [7:0] outs;  
  
    yicode tyone(ins, outs);  
    initial  
    begin  
        ins = 3'b000;  
        #100  
        ins = 3'b001;  
        #100  
        ins = 3'b010;  
        #100  
        ins = 3'b011;  
        #100  
        ins = 3'b100;  
        #100  
        ins = 3'b101;  
        #100  
        ins = 3'b111;  
        #100  
    end  
endmodule
```




3.电路分析

 

4.能耗分析 能耗大多消耗在 I/O 上

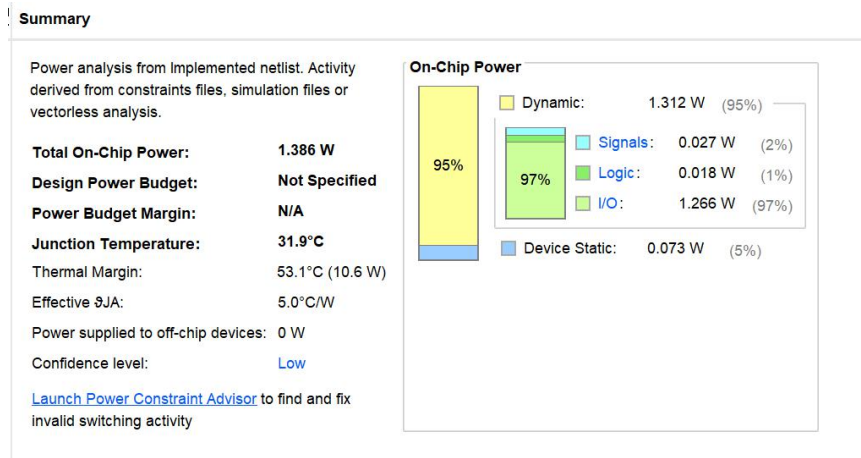

5.资源分析 LUT 消耗不多

 

三、 三位四选一数据选择器


1. 代码实现 (*en* 为控制开关, *en* 为 0 时没有输出, *w* 为选择开关)

```
module FourOne(d1, d2, d3, d4, w, f, en);  
    input [2:0]d1;  
    input [2:0]d2;  
    input [2:0]d3;  
    input [2:0]d4;  
    input [1:0]w;  
    input en;  
    output reg[2:0] f;  
    always @ (d1 or d2 or d3 or d4 or w or en)  
    begin  
        if(en==0)  
            f=0;  
        else  
            begin  
                case(w)  
                    2'b00:f=d1;  
                    2'b01:f=d2;  
                    2'b10:f=d3;  
                    2'b11:f=d4;  
                endcase  
            end  
        end  
    end
```

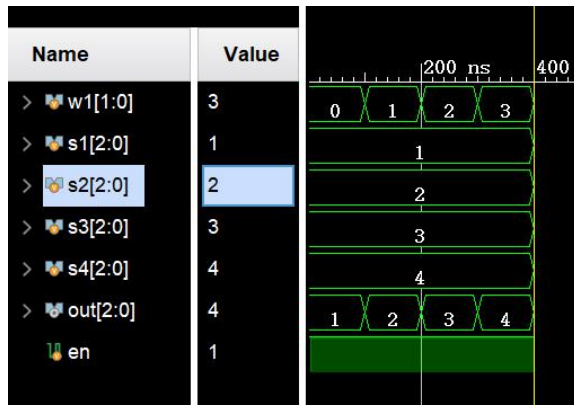
2. 仿真代码及结果

不断改变输入, 查看输出是否为预期结果

```
module try();  
    reg [1:0]w1;  
    reg [2:0] s1;  
    reg [2:0] s2;  
    reg [2:0] s3;  
    reg [2:0] s4;  
    wire [2:0] out;  
    reg en;  
    FourOne tyeone(s1, s2, s3, s4, w1, out, en);  
  
    initial  
    begin  
        s1 = 001;  
        s2 = 010;  
        s3 = 011;  
        s4 = 100;  
        w1 = 2'b00;  
        en = 1;  
        #100  
        w1 = 2'b01;  
        #100  
        w1 = 2'b10;  
        #100  
        w1 = 2'b11;  
        #100  
        $stop;  
        $finish;  
    end  
endmodule
```



3. 电路分析

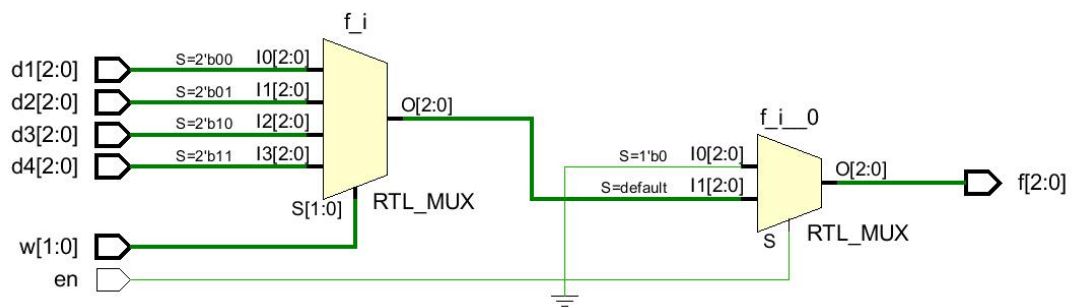

4. 能耗分析 能耗大多消耗在 I/O 上


Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 3.015 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 40.1°C
 Thermal Margin: 44.9°C (8.9 W)
 Effective θ_{JA} : 5.0°C/W
 Power supplied to off-chip devices: 0 W
 Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity


On-Chip Power

 

5. 资源分析

Summary

Resource	Utilization	Available	Utilization %
LUT	5	20800	0.02
IO	18	106	16.98

 

四、 数据分配器（四个输出端口，两位选择输入）

1. 代码实现 （D 为要输出的数据，A0,A1 为选择信号，其余为输出端口）

```
module demux(D,A0,A1,Y0,Y1,Y2,Y3);
    input [2:0] D;
    input A0,A1;
    output reg [2:0] Y0;
    output reg [2:0] Y1;
    output reg [2:0] Y2;
    output reg [2:0] Y3;
    always@(D or A0 or A1)
    begin
        case({A1,A0})
            2'b00:
                begin
                    Y0 = D; Y1 = 3'bzzz; Y2 = 3'bzzz; Y3 = 3'bzzz;
                end
            2'b01:
                begin
                    Y1 = D; Y0 = 3'bzzz; Y2 = 3'bzzz; Y3 = 3'bzzz;
                end

            2'b10:
                begin
                    Y2 = D; Y1 = 3'bzzz; Y0 = 3'bzzz; Y3 = 3'bzzz;
                end
            2'b11:
                begin
                    Y3 = D; Y1 = 3'bzzz; Y2 = 3'bzzz; Y0 = 3'bzzz;
                end
        endcase
    end
endmodule
```

2. 仿真代码及结果


```
module try();
    reg [2:0] D;
    reg A0;
    reg A1;
    wire [2:0] Y0;
    wire [2:0] Y1;
    wire [2:0] Y2;
    wire [2:0] Y3;

    demux tryone(D,A0,A1,Y0,Y1,Y2,Y3);

    initial
    begin
        D = 3'b111;
        #100
        A0 = 1'b0; A1 = 1'b0;
        #100
        A0 = 1'b1; A1 = 1'b0;
        #100
        A0 = 1'b0; A1 = 1'b1;
        #100
        A0 = 1'b1; A1 = 1'b1;
    end
endmodule
```



3. 电路分析

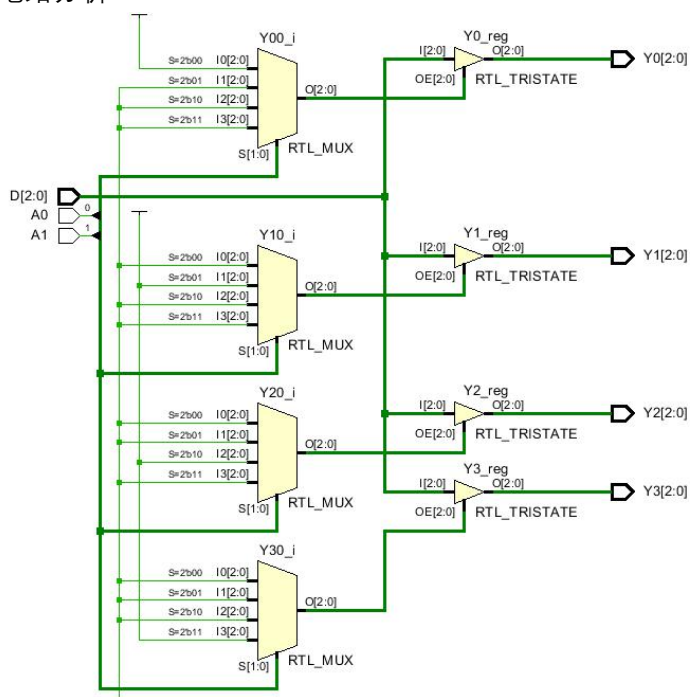

4. 能耗分析 能耗大多消耗在 I/O 上


Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.868 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 29.3°C
 Thermal Margin: 55.7°C (11.1 W)
 Effective θ_{JA} : 5.0°C/W
 Power supplied to off-chip devices: 0 W
 Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity


On-Chip Power

 

5. 资源分析

Summary

Resource	Utilization	Available	Utilization %
LUT	2	20800	0.01
IO	17	106	16.04

 

五、 数值比较器（三位）

1. 代码实现 ($A > B$ 输出 1, $A = B$ 输出 2, $A < B$ 输出 4)

```
module compare(A,B,out);
    input [2:0] A;
    input [2:0] B;
    output reg [2:0] out;


    always@(A,B)
    begin
        if(A > B)
            out <= 3'b001;
        else if(A == B)
            out <= 3'b010;
        else
            out <= 3'b100;
        end
    endmodule
```

2. 仿真代码及结果


```
module try();
    reg [2:0] A;
    reg [2:0] B;
    wire [2:0] out;

    compare tyrone(A,B,out);

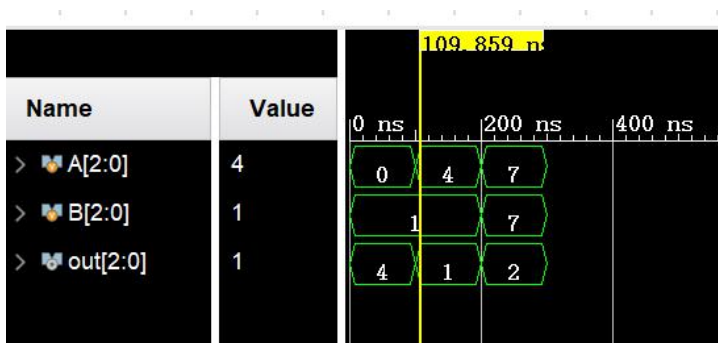    initial
    begin
        // #100 // A < B
        A = 3'b000;
        B = 3'b001;
        #100 // A > B
        A = 3'b100;
        B = 3'b001;
        #100 // A = B
        A = 3'b111;
        B = 3'b111;
        #100
        $finish;
        $stop;
    end
```



3. 电路分析

 

4. 能耗分析


Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 1.078 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 30.4°C
 Thermal Margin: 54.6°C (10.9 W)
 Effective θ_{JA} : 5.0°C/W
 Power supplied to off-chip devices: 0 W
 Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity


On-Chip Power

 

5. 资源分析

Summary

Resource	Utilization	Available	Utilization %
LUT	3	20800	0.01
IO	9	106	8.49

 

B. 时序逻辑电路

一、同步四位计数器

1. 代码实现

```
module count(cout, q, clk, clr, load, en, d);
    output reg [3:0] q; //输出
    output reg cout; //进位信号
    input clk, clr, load, en; //clr为置0信号, en为计数信号
    input [3:0] d;

    always@(posedge clk)
        begin
            if(clr)
                begin
                    q <= 0;
                end
            else if(load)
                begin
                    q <= d;
                end
            else if(en)
                begin
                    q <= q+1;
                    if(q==4'b1111)
                        begin
                            cout <= 1;
                        end
                    else
                        begin
                            cout <= 0;
                        end
                end
            else
                begin
                    q <= q;
                end
        end
endmodule
```

2. 仿真代码及结果

```

module try();
    wire [3:0] q;
    wire cout;
    reg load, clk, clr, en;
    reg [3:0] d;

    count tryone(cout, q, clk, clr, load, en, d);
    initial
    begin
        clk = 1;
        forever #50
            clk = ~clk;
    end

    initial
    begin
        clr = 1; //一开始要先将输出置0
        en = 0;
        load = 0;
        #100
        clr = 0;
        en = 1;

```

```

        clr = 0;
        en = 1;
        load = 0;
        #100
        clr = 0;
        en = 1;
        load = 0;
        #100
        clr = 1;
        en = 1;
        load = 0;
        #100
        clr = 0;
        en = 1;
        load = 0;
        #100
        load = 1;
        d = 4'b1000;
        clr = 0;
        en = 1;
        #100

```

```


$finish;

```


5. 资源分析

Summary

Resource	Utilization	Available	Utilization %
LUT	6	20800	0.03
FF	5	41600	0.01
IO	13	106	12.26

 

二、 八位二进制寄存器

1. 代码实现


```
module eightreg(out, in, clk, oe);  
    input [7:0] in;  
    input oe, clk;  
    output reg [7:0] out;  
  
    always@(posedge clk)  
        begin  
            if(oe)  
                out <= 8'bz;  
            else  
                out <= in;  
        end  
endmodule
```

2. 仿真代码及结果


```
module try( );
    reg [7:0] in;
    reg clk;
    reg oe;
    wire [7:0] out;

    eightreg tryone(out, in, clk, oe);
    initial
        begin
            clk = 1;
            forever #50 clk = ~clk;
        end
    initial
        begin
            oe = 1;
            in = 8'b00000001;
            #100
            oe = 0;
            in = 8'b00000001;
            #100
            oe = 0;
            in = 8'b00000010;

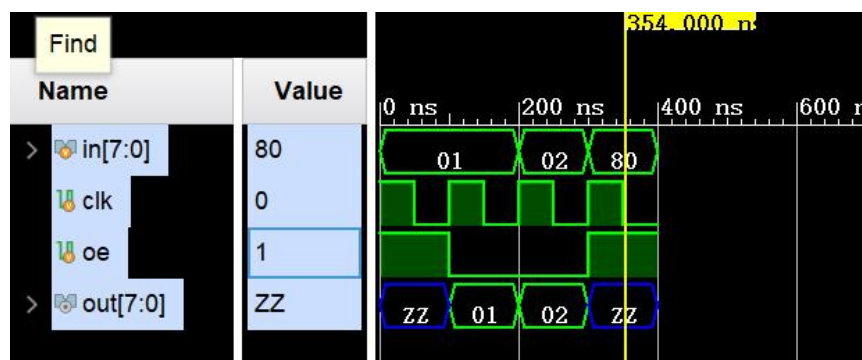            #100
            oe = 1;
            in = 8'b10000000;
            #100
            $finish;
            $stop;
        end
endmodule
```



3. 电路分析

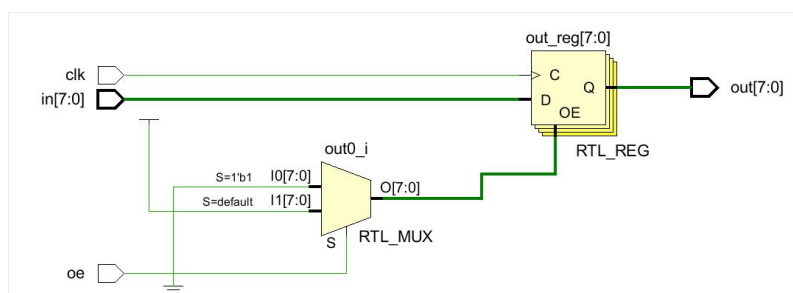


4. 能耗分析

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 1.146 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 30.7°C
 Thermal Margin: 54.3°C (10.8 W)
 Effective θ_{JA} : 5.0°C/W
 Power supplied to off-chip devices: 0 W
 Confidence level: Low
[Launch Power Constraint Advisor](#) to find and fix invalid switching activity


On-Chip Power

 

5. 资源分析

Summary

Resource	Utilization	Available	Utilization %
FF	9	41600	0.02
IO	18	106	16.98

 

三、 八位锁存器

锁存器：锁存器是电平敏感的，只要时钟信号有效，锁存器就会起作用。当 oe 为 1，锁存器工作，输出为高阻值，当 oe 为 0，g 为 1，锁存器不工作，输出等于输入。

1. 代码实现


```
module lockreg(in, out, oe, g);  
    input [7:0] in;  
    output reg [7:0] out;  
    input oe, g; //三态控制端, 控制信号  
  
    always@(*)  
    begin  
        if(oe)  
            out <= 8'bz;  
        else if(g)  
            out <= in;  
        end  
    endmodule
```

2. 仿真代码及结果


```
module try();  
    reg [7:0] in;  
    reg eo, g;  
    wire [7:0] out;  
  
    lockreg tryone(in, out, eo, g);  
  
    initial  
    begin  
        eo = 1;  
        g = 0;  
        in = 8'b00000001;  
        #100  
        eo = 0;  
        g = 1;  
        in = 8'b00000001;  
        #100  
        eo = 0;  
        g = 1;  
        in = 8'b00000010;  
        #100  
        eo = 1;  
        g = 0;  
        #100  
        in = 8'b00000100;  
        #100  
        $finish;  
        $stop;  
    end  
endmodule
```




3. 电路分析

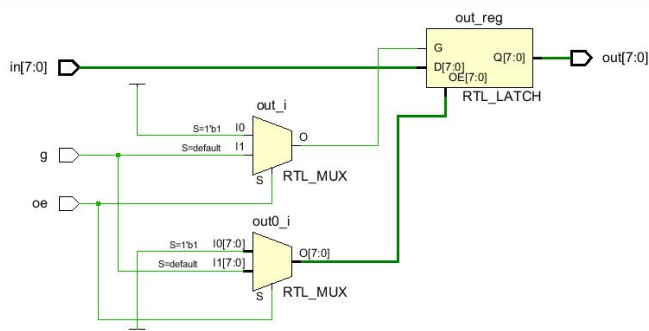

4. 能耗分析 signals 也是消耗了一部分能耗

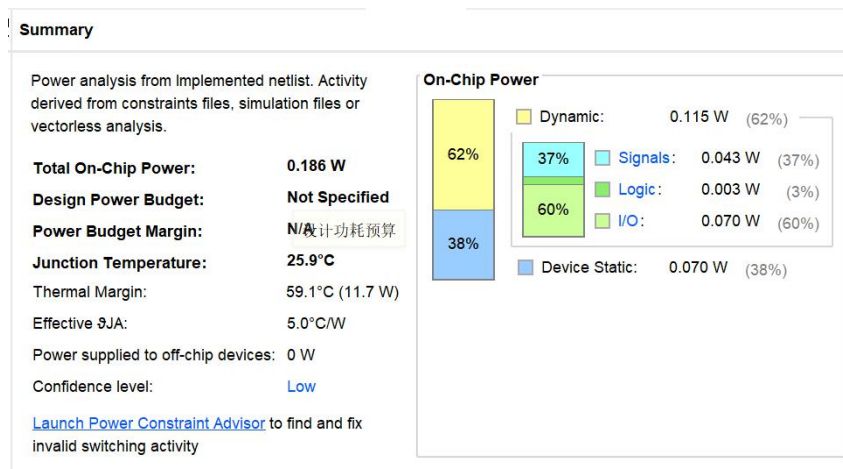

5. 资源分析

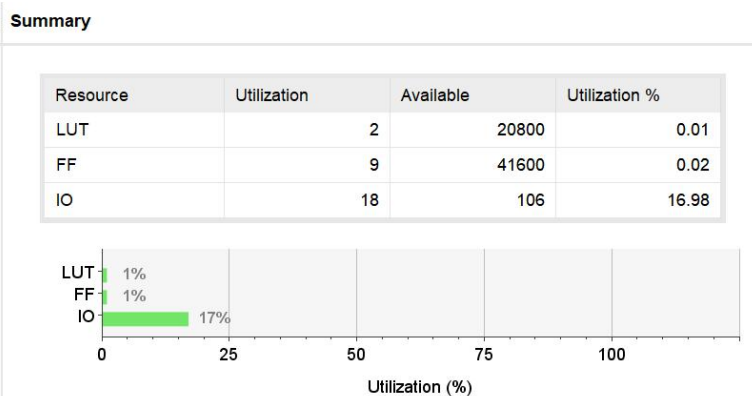

四、 存储器

建立一个 4 个 8 位寄存器，choice 代表选择，为 1 时为写入数据状态，为 0 时为读取所存储的数据的状态。num 代表选择写入或读取哪一个数据。

1. 代码实现

```
module store(data_1, data_2, data_3, data_4,choice,num,out,clk);
    input [7:0] data_1;
    input [7:0] data_2;
    input [7:0] data_3;
    input [7:0] data_4;
    input clk;
    reg [7:0] store_1;
    reg [7:0] store_2;
    reg [7:0] store_3;
    reg [7:0] store_4;
    input choice;
    input [1:0]num;
    output reg [7:0] out;

    always@(posedge clk)
        begin
            if(choice)
                begin
                    case(num)
                        2'b00: store_1 = data_1;
                        2'b01: store_2 = data_2;
                        2'b10: store_3 = data_3;
                        2'b11: store_4 = data_4;
                    endcase
                end
            else
                begin
                    case(num)
                        2'b00: out = store_1;
                        2'b01: out = store_2;
                        2'b10: out = store_3;
                        2'b11: out = store_4;
                    endcase
                end
            end
        end
endmodule
```

2 仿真文件及结果

```

module try();

    reg [7:0] data_1;
    reg [7:0] data_2;
    reg [7:0] data_3;
    reg [7:0] data_4;
    reg clk;
    reg choice;
    reg [1:0] num;
    wire [7:0] out;

    store tryone(data_1, data_2, data_3, data_4, choice, num, out, clk);

    initial
    begin
        clk = 1;
        forever #50 clk = ~clk;
    end

    initial
    begin
        data_1 = 8'b00000001;

```

```


        data_2 = 8'b00000010;
        data_3 = 8'b00000100;
        data_4 = 8'b00001000;
        choice = 1;
        num = 2'b00;
        #100;
        choice = 1;
        num = 2'b01;
        #100
        num = 2'b10;
        #100
        num = 2'b11;
        #100
        choice = 0;
        num = 2'b00;
        #100
        num = 2'b01;
        #100
        num = 2'b10;
        #100
        num = 2'b11;
        #100

```


```

        $finish;
        $stop;
    end
endmodule

```

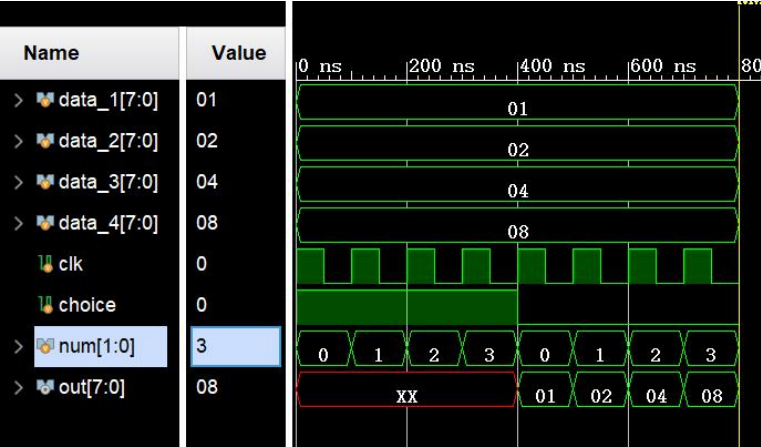

3 电路分析

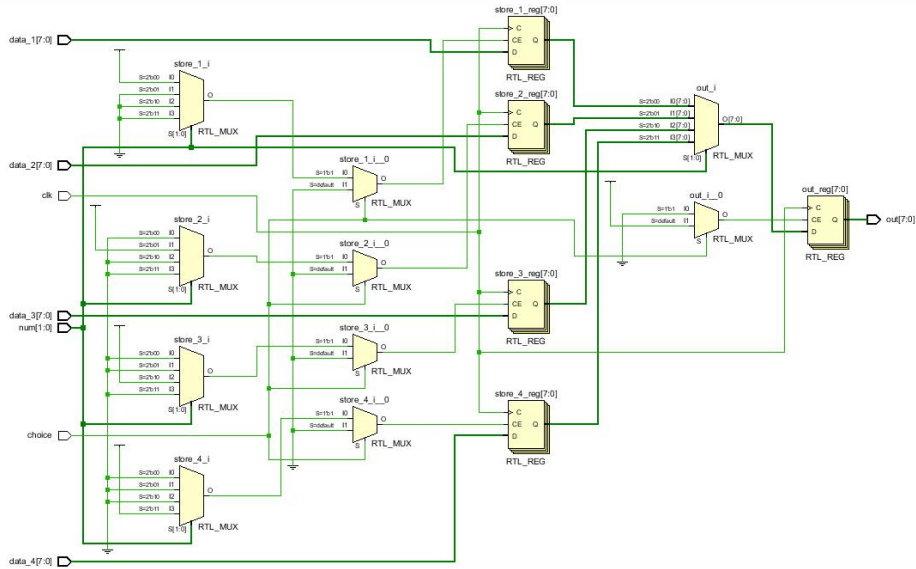

4 能耗分析


Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 3.66 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 43.3°C
Thermal Margin: 41.7°C (8.3 W)
Effective θ_{JA} : 5.0°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

5 资源分析

Summary

Resource	Utilization	Available	Utilization %
LUT	13	20800	0.06
FF	40	41600	0.10
IO	44	106	41.51

